 



### Full Adder:

In this article we write Verilog code for full adder that adds three inputs and produces two outputs. The first two inputs are A and B, and the third input is an input carry as C-IN. The output carry is designated as C-OUT and the normal output is designated as S which is SUM. The C-OUT is also known as the majority 1's detector, whose output goes high when more than one input is high. A full adder logic is designed in such a manner that can take eight inputs together to create a byte-wide adder and cascade the carry bit from one adder to another. we use a full adder because when a carry-in bit is available, another 1-bit adder must be used since a 1-bit half-adder does not take a carry-in bit. A 1-bit full adder adds three operands and generates 2-bit results.

### Logic Symbol:



### Logic Circuit:

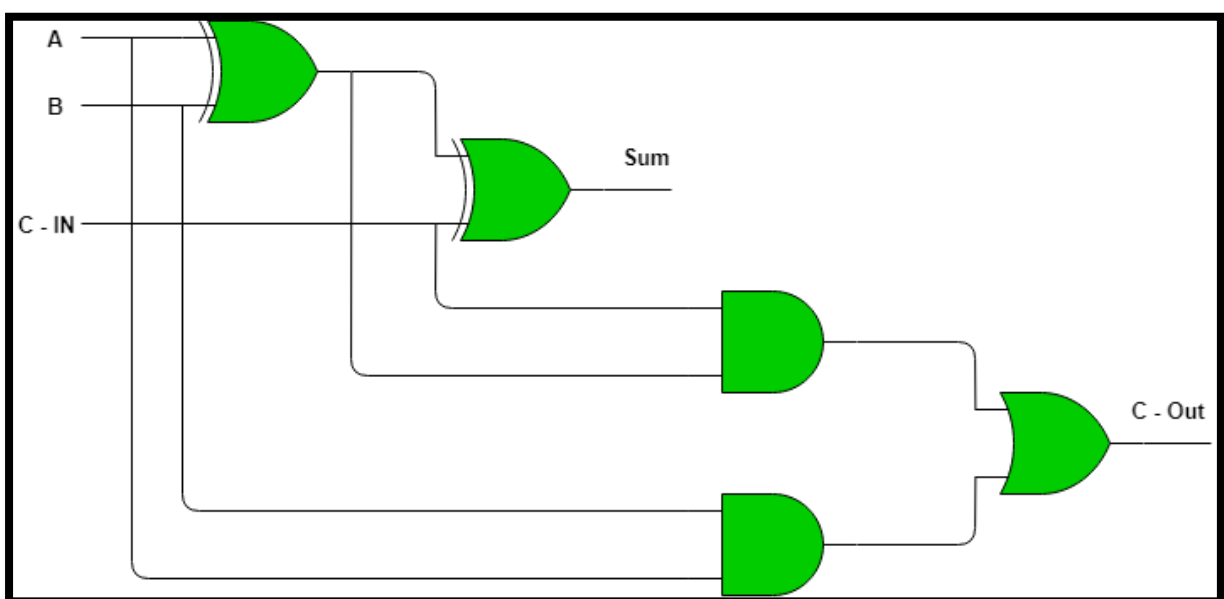

**Truth Table:**

Inputs			Outputs	
A	B	C – IN	Sum	C – Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Verilog Code:**

```
module full_adder(a,b,c,s,c_out);
input a,b,c;
output s,c_out;
wire w1,w2,w3;
xor(w1,a,b);
and(w2,a,b);
and(w3,c,w1);
xor(s,w1,c);
or(c_out,w2,w3);
endmodule
```


**Testbench:**

```
module full_adder_tb();
reg a,b,c;
wire s,c_out;
full_adder f1(a,b,c,s,c_out);
initial
begin
a=0;b=0;c=0;
#100
a=0;b=0;c=1;
#100
a=0;b=1;c=0;
#100
a=0;b=1;c=1;
#100
a=1;b=0;c=0;
#100
a=1;b=0;c=1;
#100
a=1;b=1;c=0;
#100
a=1;b=1;c=1;
#100 $finish;
end
initial
begin
$display("\t\t\t\tTime \ta \tb \tc \ts \tc_out");
$monitor($time,"\t",a,"\t",b,"\t",c,"\t",s,"\t",c_out);
end
endmodule
```

## Simulation:



## RTL Design:

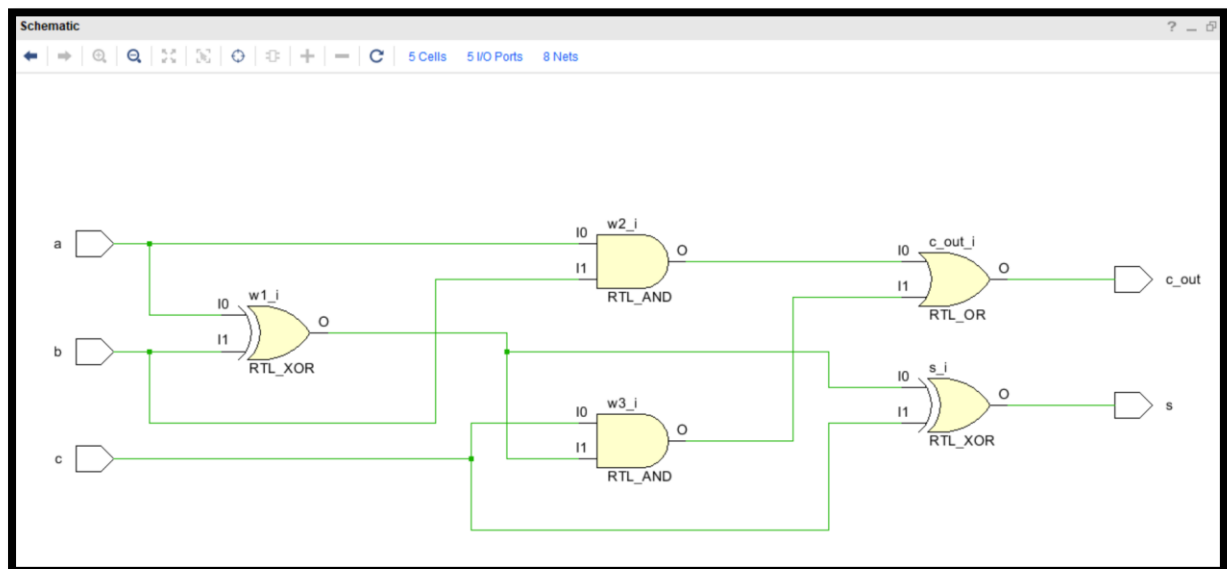

## Tcl Console:

```
Tcl Console x Messages Log
INFO: [USF-XSim-69] 'elaborate' step finished in '2' seconds
Vivado Simulator 2018.2
Time resolution is 1 ps

Time    a    b    c    s    c_out
0       0    0    0    0    0
100     0    0    1    1    0
200     0    1    0    1    0
300     0    1    1    0    1
400     1    0    0    1    0
500     1    0    1    0    1
600     1    1    0    0    1
700     1    1    1    1    1

$finish called at time : 800 ns : File "E:/Vivado/Verilog/Gat
```

## Application:

**1.Arithmetic circuits:** Full adders are utilized in math circuits to add twofold numbers. At the point when different full adders are associated in a chain, they can add multi-bit paired numbers.

**2.Data handling:** Full adders are utilized in information handling applications like advanced signal handling, information encryption, and mistake rectification.

**3.Counters:** Full adders are utilized in counters to addition or decrement the count by one.

**4.Multiplexers and demultiplexers:** Full adders are utilized in multiplexers and demultiplexers to choose and course information.

**5.Memory tending to:** Full adders are utilized in memory addressing circuits to produce the location of a particular memory area.

**6.ALUs:** Full adders are a fundamental part of Number juggling Rationale Units (ALUs) utilized in chip and computerized signal processors.