
#### **Ripple Carry Adder:**

A Ripple-Carry Adder is defined as a method of constructing an N-bit carry propagate adder by chaining together N full adders, where the carry out of one stage acts as the carry in of the next stage. This approach is modular and regular but can be slow for large N due to the carry rippling through the chain. But in our case, we want to design 4-bit ripple carry adder so we did not take C in and use only one half adder and three full adder.


## Circuit Diagram:

 


```
Verilog Code:
                                             Testbench:
moduleripple carry 4bit adder(a,b,s,c out);
                                             module
input [3:0] a,b;
                                             ripple carry 4bit adder tb();
                                             reg [3:0] A,B;
output [3:0]s;
output c out;
                                             wire [3:0] S;
wire c1,c2,c3;
                                             wire C out;
                                             ripple carry 4bit adder
half adder h1(a[0],b[0],s[0],c1);
full adder f1(a[1],b[1],c1,s[1],c2);
                                             A1(A,B,S,C \text{ out});
full_adder f2(a[2],b[2],c2,s[2],c3);
                                             initial
full adder f3(a[3],b[3],c3,s[3],c out);
                                             begin
endmodule
                                             A=4'd2;B=4'd3;
                                             #100
                                             $display("Time=%d A=%b B=%b
                                             S=\%b
                                             C out=\%b\n'',$time,A,B,S,C out);
                                             A=4'd9;B=4'd9;
                                             #100
                                             $display("Time=%d A=%b B=%b
                                             C out=\%b\n",$time,A,B,S,C out);
                                             A=4'd5;B=4'd8;
                                             #100
                                             $display("Time=%d A=%b B=%b
                                             S=\%b
                                             C out=\%b\n'',$time,A,B,S,C out);
                                             #100 $stop;
                                             end
                                             endmodule
```

#### Verilog Code for full adder: Verilog Code half adder: module half\_adder(a,b,s,c); module full\_adder(a,b,c,s,c\_out); input a,b; input a,b,c; output s,c; output s,c out; xor(s,a,b);wire w1,w2,w3; and(c,a,b); xor(w1,a,b);endmodule and(w2,a,b); and(w3,c,w1); xor(s,w1,c);or(c\_out,w2,w3); endmodule

## **Simulation:**

 

# RTL design:

 

### **Tcl Console:**