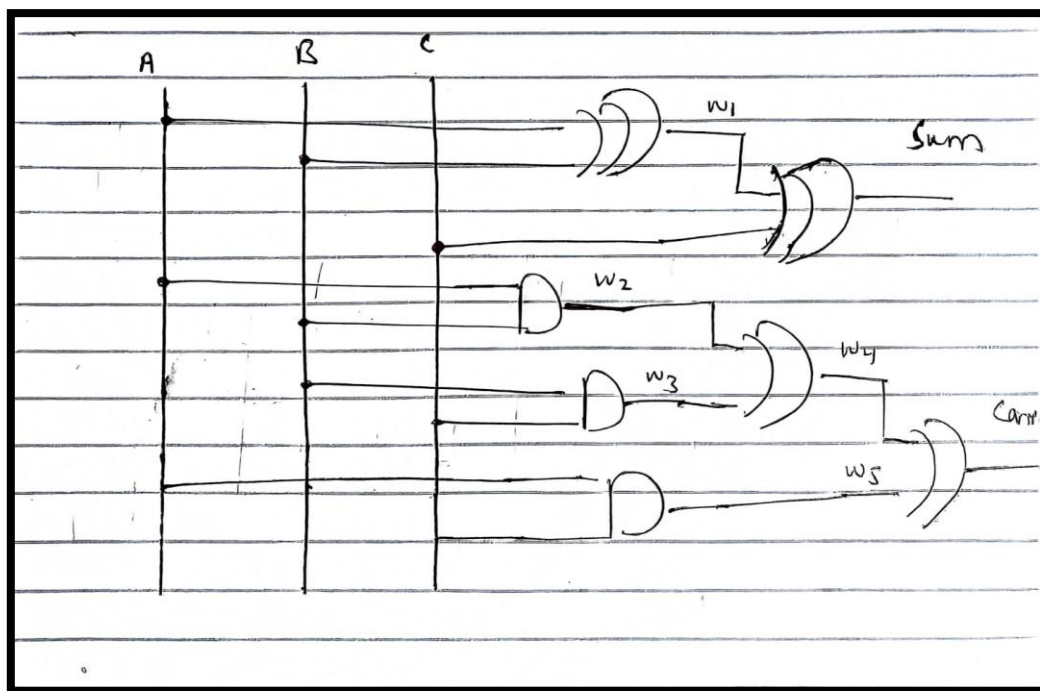


### Full adder:

Full Adder is the adder that adds three inputs and produces two outputs. The first two inputs are A and B, and the third input is an input carry as C-IN. The output carry is designated as C-OUT and the normal output is designated as S which is SUM. The C-OUT is also known as the majority 1's detector, whose output goes high when more than one input is high. A full adder logic is designed in such a manner that can take eight inputs together to create a byte-wide adder and cascade the carry bit from one adder to another. we use a full adder because when a carry-in bit is available, another 1-bit adder must be used since a 1-bit half-adder does not take a carry-in bit. A 1-bit full adder adds three operands and generates 2-bit results.

### Logic Circuit:



### Truth Table:

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


```

module full_adder(a,b,c,s,c_out);
input a,b,c;
output s,c_out;
wire w1,w2,w3,w4;
// for sum
assign w1=a^b;
assign s=w1^c;
// for carry
assign w2=a&b;
assign w3=b&c;
assign w4=a&c;
assign c_out=w2|w3|w4;
endmodule


```

```
module full_adder_tb();  
    reg x,y,z;  
    wire s,c_out;  
    full_adder f1(x,y,z,s,c_out);  
    initial  
        begin  
            x=0;y=0;z=0;  
            #100  
            x=0;y=0;z=1;  
            #100  
            x=0;y=1;z=0;  
            #100  
            x=0;y=1;z=1;  
            #100  
            x=1;y=0;z=0;  
            #100  
            x=1;y=0;z=1;  
            #100  
            x=1;y=1;z=0;  
            #100  
            x=1;y=1;z=1;  
            #100 $finish;  
        end  
    initial  
        begin  
            $display("\t\t\t\ttime\tx\ty\tz\t\t\tc_out");  
            $monitor($time,"\t",x,"\t",y,"\t",z,"\t",s,"\t",c_out);  
        end  
endmodule
```


### Sources:

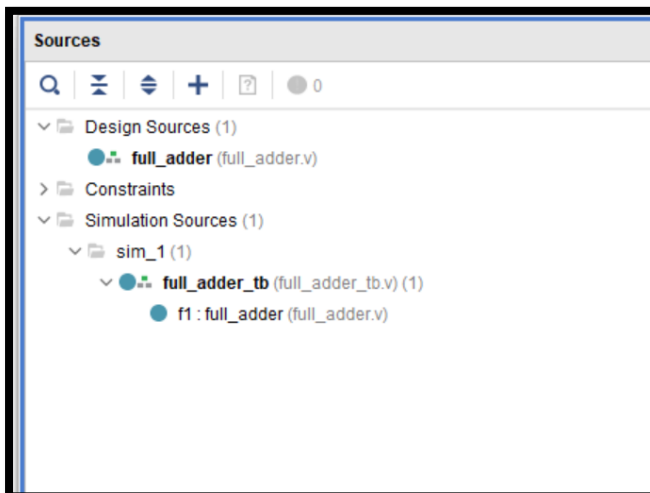


## Simulation:

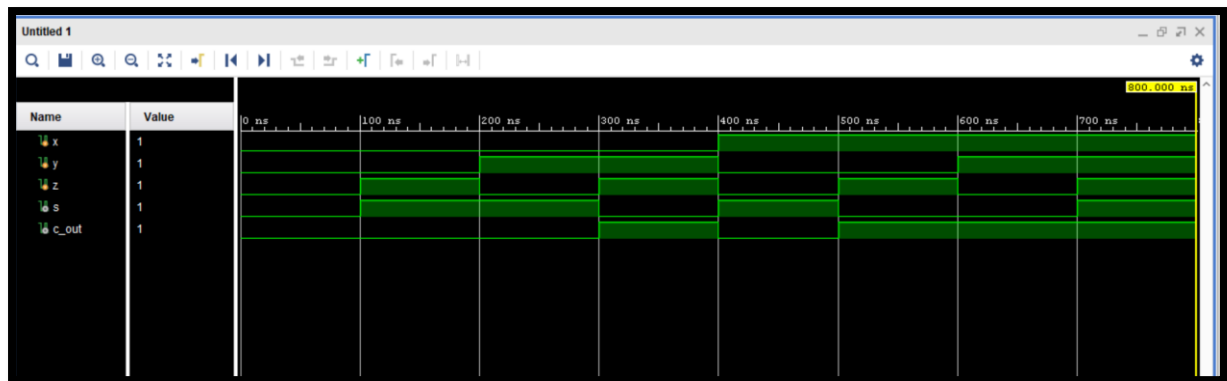

## RTL Design:

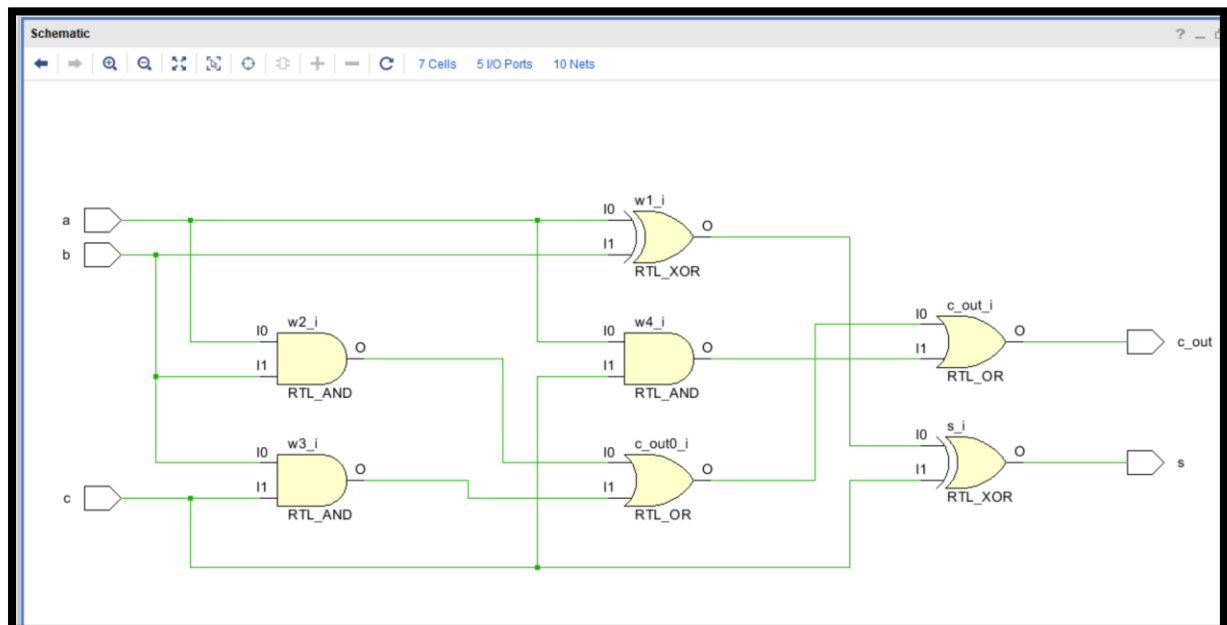

## Tcl Console:

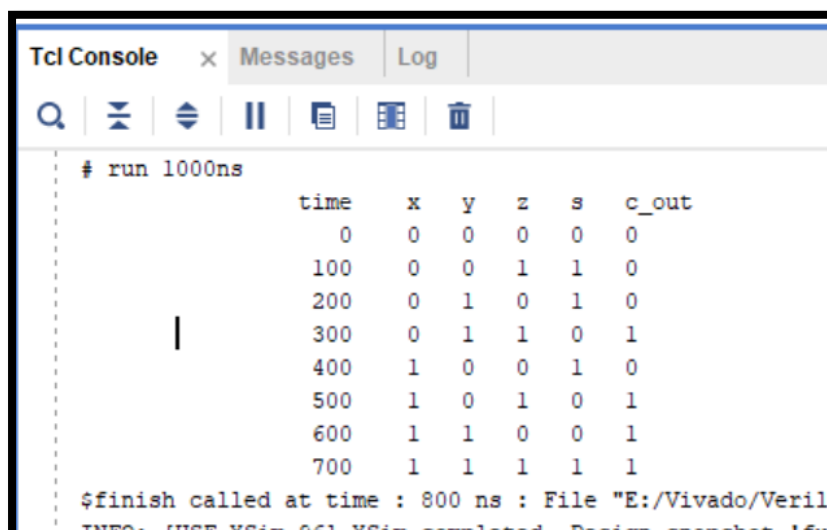

## Application:

**1.Arithmetic circuits:** Full adders are utilized in math circuits to add twofold numbers. At the point when different full adders are associated in a chain, they can add multi-bit paired numbers.

**2.Data handling:** Full adders are utilized in information handling applications like advanced signal handling, information encryption, and mistake rectification.

**3.Counters:** Full adders are utilized in counters to addition or decrement the count by one.

**4.Multiplexers and demultiplexers:** Full adders are utilized in multiplexers and demultiplexers to choose and course information.

**5.Memory tending to:** Full adders are utilized in memory addressing circuits to produce the location of a particular memory area.

**6.ALUs:** Full adders are a fundamental part of Number juggling Rationale Units (ALUs) utilized in chip and computerized signal processors.